


# ASSIGNMENT 2

## AIM:


To design LPF, HPF and BPF Circuits in NGSPICE.

## CIRCUIT:


1. LPF:

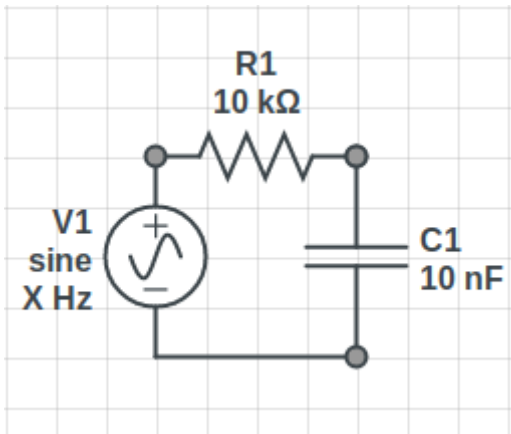

2. HPF:

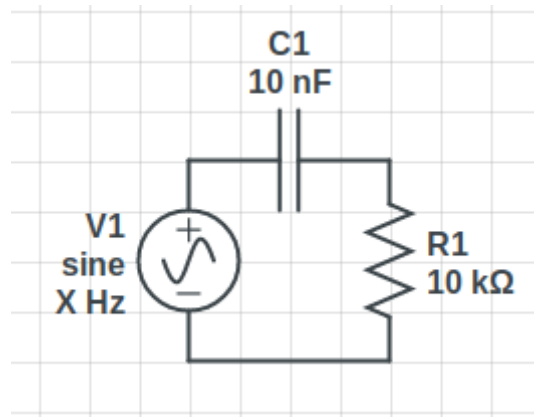


3. BPF:

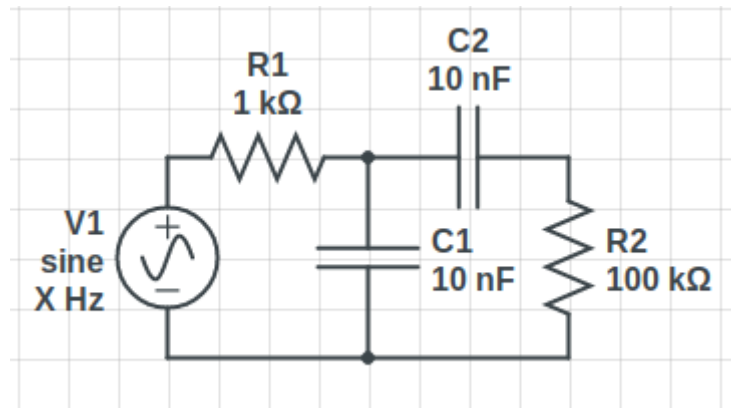


# OBSERVATIONS:


## 1. Low Pass Filter AC analysis:

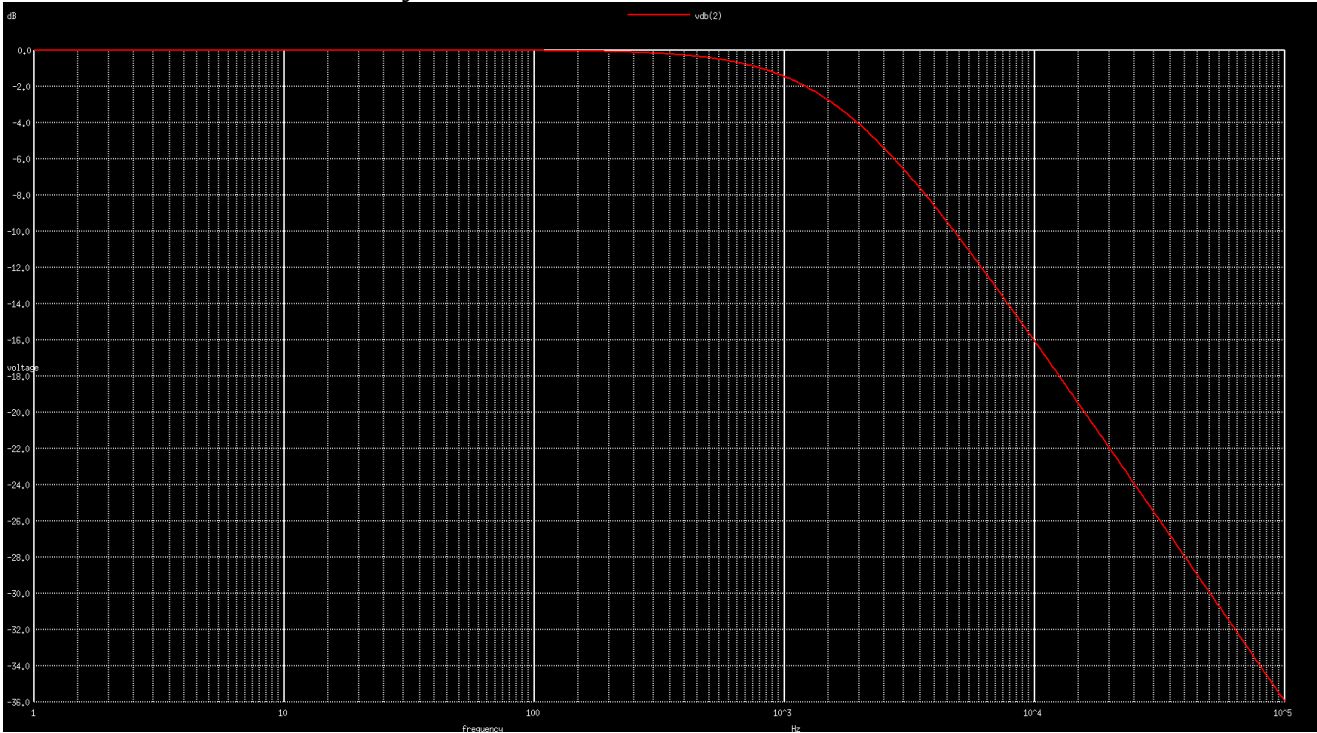

## 2. High Pass Filter AC analysis:

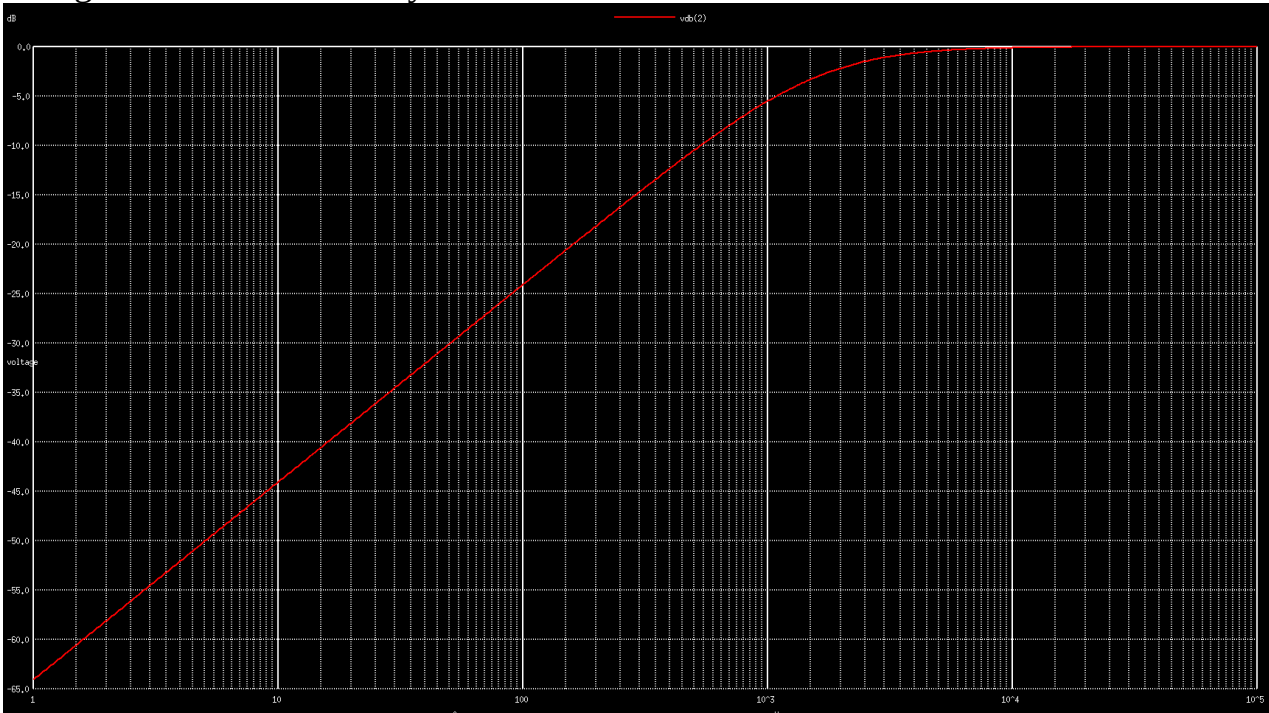

### 3. Band Pass Filter AC analysis:

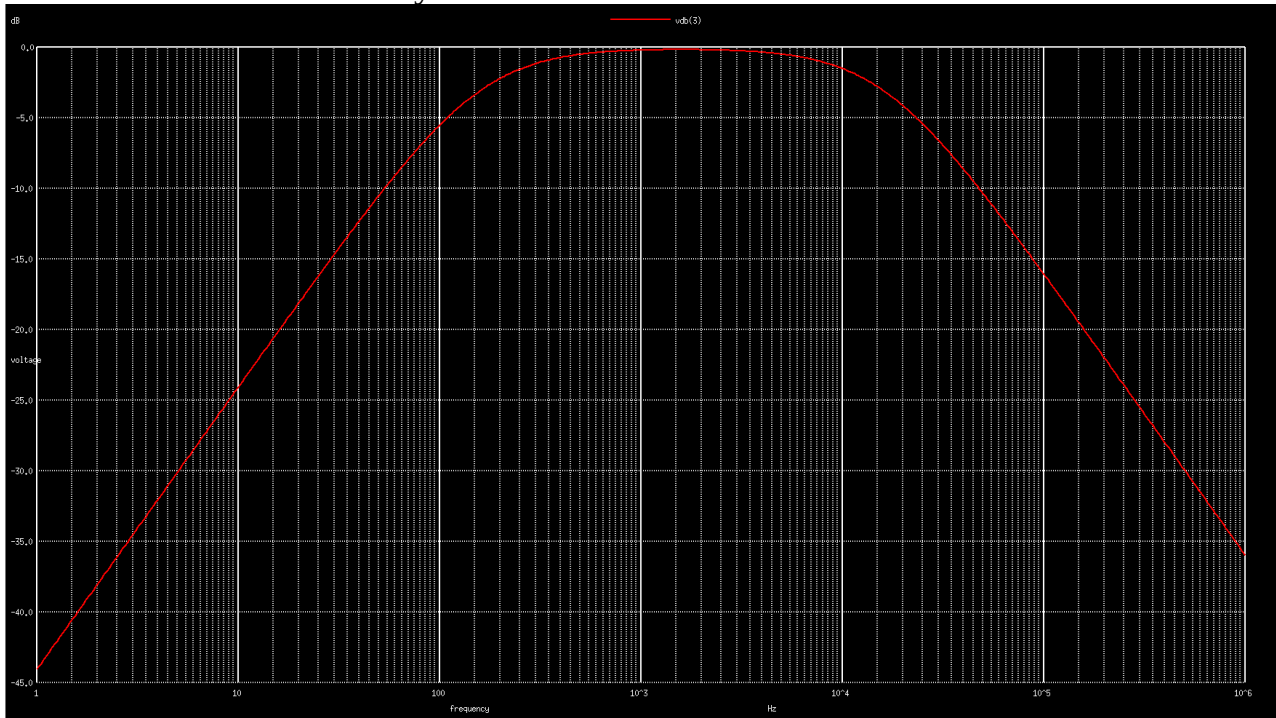

### **CONCLUSION/RESULT:**

1. The LPF cut off is kept at ~1.6 KHz using an RC circuit with  $R_1=10k$  and  $C_1=10n$ .
2. The HPF cut off is kept at ~1.6 KHz using an RC circuit with  $R_1=10k$  and  $C_1=10n$ .
3. The BPF cut off is kept at ~160 Hz - ~160 KHz using two RC circuits(an LPF and an HPF) using  $R_1=1k$ ,  $C_1=10n$  and  $R_2=100k$ ,  $C_2=10n$