

Experiment -2

1.1 Aim

Design of Single stage CS amplifier (i) with resistive load (ii) active load

1.2 Circuit Description

 


Fig.1.1 CS amplifier with resistive load

In fig.1.1 a simplest form of amplifier is shown. It mainly consists a nMOS, connected in common source configuration. Actually MOS converts gate volte to current i.e. $g_m V_{gs}$. To get this current in the form of voltage, we attach a resistor and across it we got the corresponding voltage. Here output resistance will be R_d parallel with r_{ds} .

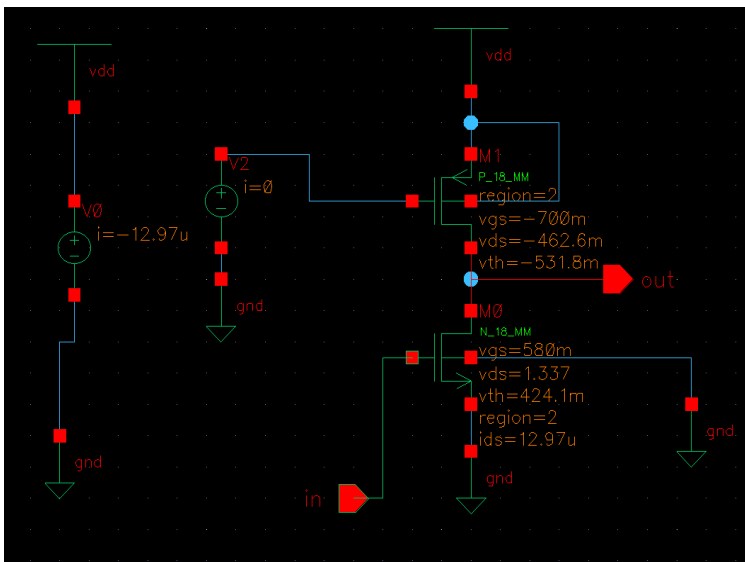


Fig.1.2. CS amplifier with active load

CS source amplifier with active load is shown in figure 1.2, which have output resistance of $r_{ds}/2$ because two r_{ds} term will come in parallel. As a load we are using pMOS because it is easier for a PMOS to make current source while connected with VDD.

1.3 Theory

- It has very high input impedance; relatively high gain, low noise, speed, and simplicity, common source amplifiers find different applications from sensor signal amplification to RF low-noise amplification [1].
- It provides 180° phase shift at the output while input is applied to gate and output is taken from the drain terminal [2].
- Being a single stage amplifier it doesn't have much gain but swing is high. These are always stable systems.
- In general its gain is $g_m \cdot R_{out}$
- It has one dominant pole at the output and one non-dominant pole at the input. With this it also has one right hand side zero [3].

1.4 Design, analysis and calculation

Suppose we want to design it for maximum voltage. Consider over drive voltage – 0.2 V and assume (W/L) is 2.

Now using

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

Calculate I_D

$$I_D = 10.8 \text{ uA}$$

$$A_v = g_m \cdot (R_D \parallel r_{ds})$$

If R_D is chosen to be equal to r_{ds} , then effective r_{ds} will become half

And now, using formula of gain, $A_v = \sqrt{2I_{D1} \mu_n C_{ox} \frac{W}{L}} \cdot (1/\lambda I_{D1})/2$ gain can be calculated theoretically

$$A_v = 10$$

But as we know r_{ds} is very high and if we choose R_D equal to r_{ds} then it will take all the voltage at drain and will allow only a very small v_{ds} .

To fulfill this condition we can go for active load.

In case of active load $R_{out} = r_{ds} \parallel r_{ds}$ and it will increase the gain.

$$A_v = g_m \cdot (r_{ds} \parallel r_{ds})$$

1.5 Observation

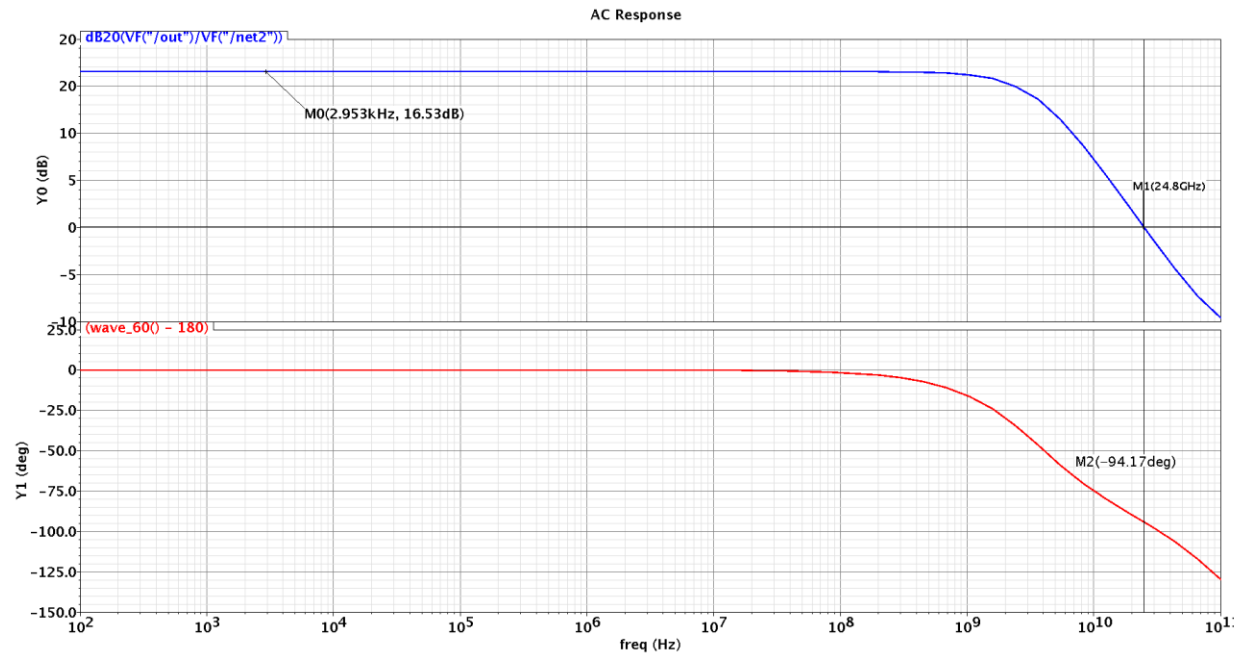


Fig.1.3 Frequency response of CS with resistive load

 


Fig. 1.4. Output voltage swing of CS with resistive load

- Fig.1.3 shows the frequency response of CS amplifier in which it clear from the plot that gain is 16.53dB ≈ 6.7 . We have calculated it as 10 but we could achieve it 6.7.
- It has a phase margin of 86° which means the system is highly stable.
- GBW of the system is 24 GHz and the 3dB frequency is 1 GHz.
- 1 **dB compression point it at 11 GHz frequency**, see from figure 1.3.
- This system has a great swing. From calculation it is V_{dd} to V_{ov} i.e. 1.8V to 0.2V but from figure 1.4 it is peak to peak 1.7 V

 


Fig.1.5. Frequency response CS with active load

 


Fig.1.6. Output voltage swing of CS with active load

- It is clear that the gain of using active load with CS increases its gain. Form figure 1.5, gain is 21.39 dB ≈ 11.73 .

- Phase margin almost remains same, in this case it is 89° .
- GBW has reduced to 7.6 GHz and so the 3dB bandwidth.
- 1 dB compression point is at 120 MHz.
- In this case swing becomes somewhat poor compare to previous case. It is because theoretically $V_{\max} = V_{DD} - V_{ov} = 1.6 \text{ V}$ and $V_{\min} = 0.2 \text{ V}$. From figure 1.6 peak to peak swing is 1.65 V

 


Fig. 1.7. Output voltage to input voltage curve has been drawn

From here also we can estimate the swing of the cs amplifier. We need to look for $\text{slop} = 1$ at this transfer curve. It is drawn here just to verify the swing values.

1.6 Conclusion

- Gain of CS amplifier is very small.
- This kind of system is highly stable as phase margin is close to 90° .
- 1 dB compression point also reduces after using active load with CS.

TABLE I

Parameter	Calculated	Simulated
A_v	10	7.6
I_d	10.80 μA	11 μA
P-P Swing (resistive load)	1.6 V	1.7V
P-P Swing (active load)	1.4 V	1.65V

- Gain CS with active load is more as compare to CS with resistive load.

- Swing of CS with active load is less compare to CS with resistive load.
- Frequency response of CS amplifier gives one dominant pole at output.
- These kind of amplifiers are not sufficient, therefore we move towards cascode , folded and other structur.

Reference-

[1]B. Razavi, “Design of Analog CMOS Integrated Circuits”, Tata McGraw Hill edition, 2002.

[2]Willy M. C. Sansen,”Analog Design Essentials” Springer; 1st ed. 2006

[3] Philip E. Allen and Douglas R. Holberg,”CMOS Analog Circuit Design”, Oxford University Press,2004