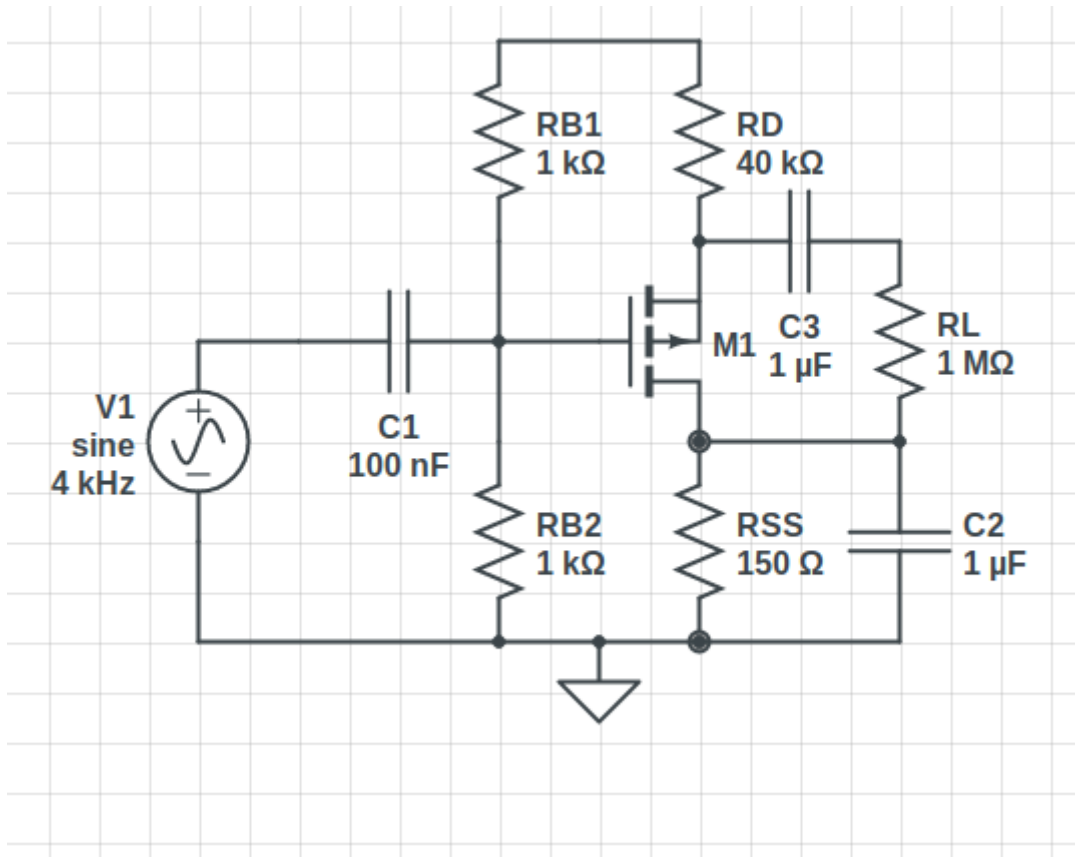


ASSIGNMENT 8


AIM:

To design an NMOS amplifier with voltage divider biasing.

CIRCUIT:



OBSERVATIONS: Without Load resistance.

 


V_{out} vs t

Data

```
No. of Data Rows : 50001
vmax                = 2.557116e+00 at= 6.607528e-04
vmin                = 2.480348e+00 at= 7.857528e-04
vmax-vmin = 7.676800e-02
```

We see that $V_{in} = 50\text{mV}_{pp}$, we have $V_{out} \sim 76\text{mV}_{pp}$, hence we have a gain of ~ 1.536

With $R_L = 1\text{M}\Omega$

 


Data -

```
No. of Data Rows : 50001
vmax                = 3.705712e-02 at= 6.607428e-04
vmin                = -3.680028e-02 at= 7.857328e-04
vmax-vmin = 7.385740e-02
```

Gain ~ 1.4772


$R_L = 50\text{K}\Omega$
 
```
No. of Data Rows : 50001
vmax                = 2.141218e-02 at= 9.105828e-04
vmin                = -2.146479e-02 at= 5.355828e-04
vmax-vmin = 4.287697e-02
```



Gain ~ 0.8576

RL = 5KOhm

 


Data

```
No. of Data Rows : 50001
vmax                =  4.283001e-03 at=  9.104028e-04
vmin                = -4.313592e-03 at=  5.354028e-04
vmax-vmin = 8.596593e-03
```

Gain ~ 0.172

RL = 1KOhm

 

Data

```
vmax      = 9.401780e-04 at= 9.103628e-04  
vmin      = -9.471151e-04 at= 5.353728e-04  
vmax-vmin = 1.887293e-03
```

Gain ~ 0.378

CONCLUSION:

We find that for lower Load Resistance (RL), the gain decreases.